Student's Name:

Introduction to circuit analysis


Homework 6 – Source Conversion and Superposition Theorem

Instructions:


- YOU HAVE TO SHOW ALL WORK IN ORDER TO RECEIVE FULL CREDIT
- All answer must be in engineering notation rounded off to the hundredth

------ Homework Starts Here ------

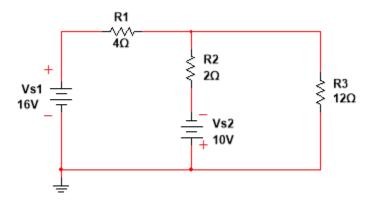
1) Use superposition theorem to the voltage and current across R₁



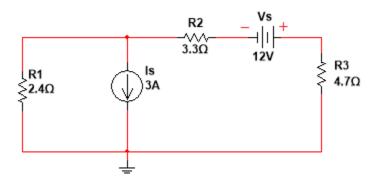2) Use *superposition theorem* to the voltage across R_3



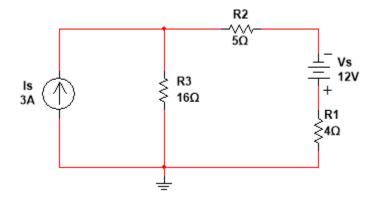3) Use **source conversion** to find the voltage and current across R_3



4) Use $source\ conversion$ to find the current and voltage through R_1

